

BUILD A HEADPHONE AMPLIFIER FOR YOUR GUITAR

Prepared by: David Lee Kean Chuong

ABSTRACT

The project title of this project is Build a Headphone Amplifier for Your Guitar. I got this project title from the magazine Popular Electronics in March 1995 issue from the Information Service Department. This project report gives you the circuit descriptions about the principle of operation of the circuit. It also contains the schematic diagram and block diagram of the circuit, with the aid of block diagram makes you understand better how it works. Each part of the device as well as the list of the components is stated properly and provided.