

3-LED LOGIC PROBE

Prepared by: Lim Yeen Chen

ABSTRACT

This text provides information to the making of the 3-LED Logic Probe circuit. Due to its convenience in handling and easy detection in IC fault, it also comes in three LEDs readily visible for the indication of high to low level changes in logic state. It also comes with a simple block diagram to reinforce the understanding of the key description of the circuit.