## 100W STEREO POWER AMPLIFIER WITH SPEAKER PROTECTOR

Prepared by: Von Sherh Huan @ Victor

## ABSTRACT

This is a project report that provides the clear information of the 100 W stereo power amplifier with speaker protector. The project report covers the contents, the list of illustrations which show the circuit diagram, block diagram and figures which able to make readers more understanding the content and description of my project report.

Besides, the body part of my project report contains the construction where there will be a detailed description on how is the prototype is being done. Furthermore, project report contains the result and analysis of my project title. There I have inserted the circuit diagrams and the explanation of the circuits as well as the outcome of each part of the circuit. In addition, I have also explained the operation of my project title as well as the function of the electronics component.

Finally, conclusion to conclude every study, analysis, and work during the process of doing the project title is included inside this project report as well as the references where I could get some useful information that may help in my project. I also have put the schedule of my project and the data sheet of the components on the appendix.