

# TONAL VOLTMETER

Prepared by: Wee Chze Siong

## ABSTRACT

---

This report will give you a complete description of my circuit and how it works. I will also introduce you to the internal operations of the IC4046 CMOS and the functions of the other components. As my circuit is quite simple, I will explain the modifications that I have made on this circuit.

All of my explanations will be supported by illustrations that serve to provide you with a clearer understating of my project.